



PROGRAMMABLE LOGIC DEVICES

Electronic and Communication Engineering Department

Lec2: FPGA Structure

Dr. Wahhab R. Mousa

wahhab.albazrqa@uokufa.edu.iq



Contents

- Introduction
- FPGA structure
- Altera DE1 SoC board
- Summary

COMPUTATIONAL STRUCTURE






Introduction

- **Programmable Logic Devices (PLDs)** is universal logic implementers in the sense that they can be configured (actually programmed) by the user to perform a variety of specific logic functions.



WHY PLDS:

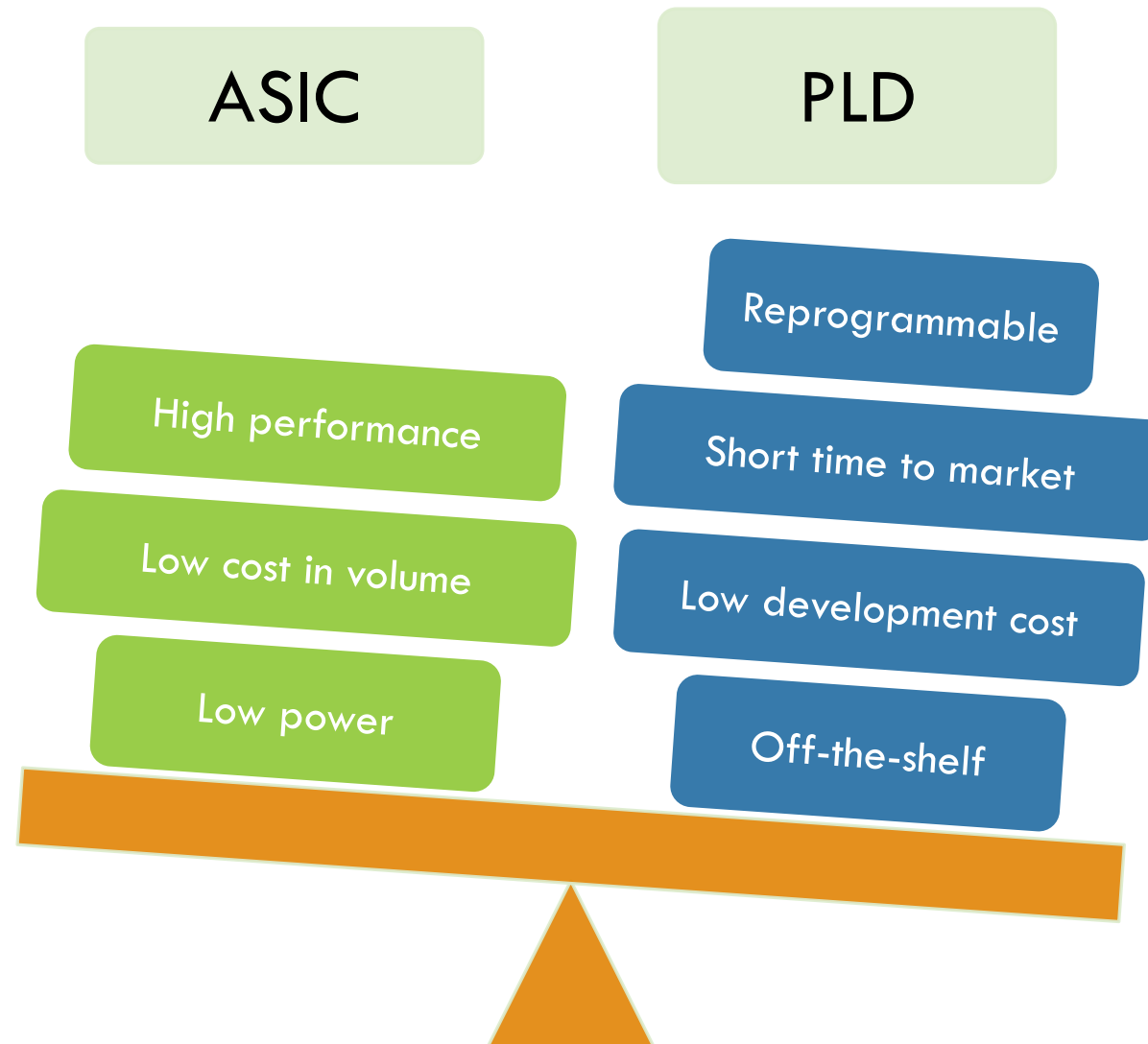

COMPUTATIONAL STRUCTURE

WHY PLDS:

 
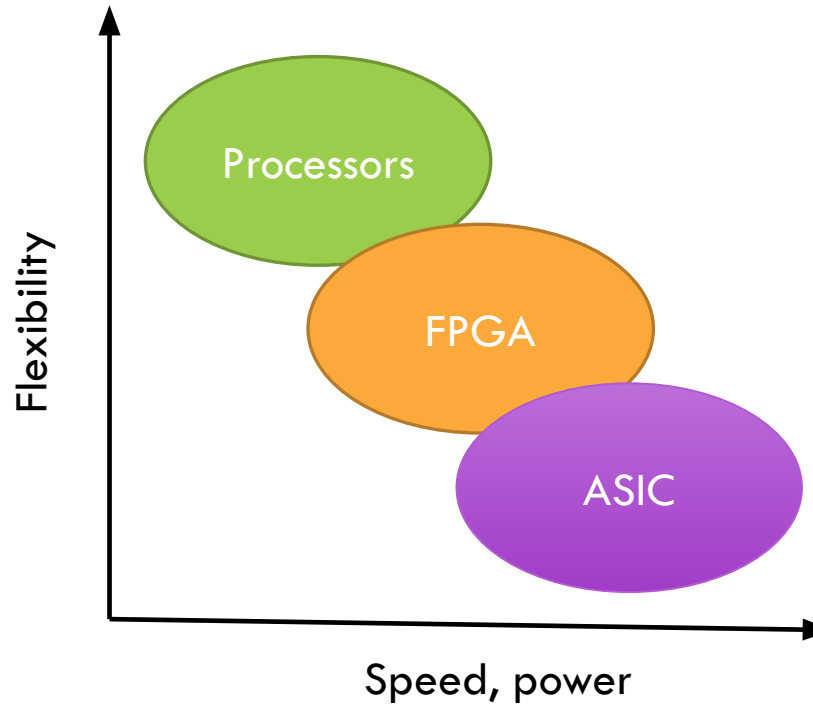
- Processors:
 - Flexibility in the programs
- ASIC (App Specific IC)
 - No flexibility
- FPGA
 - Device re-programmability



FPGA priceable


- A **Field-Programmable Gate Array (FPGA)** is an integrated circuit that can be configured by the user to emulate any digital circuit as long as there are enough resources
- An FPGA can be seen as an array of Configurable Logic Blocks (CLBs) connected through programmable interconnect (Switch Boxes)

FPGA STRUCTURE

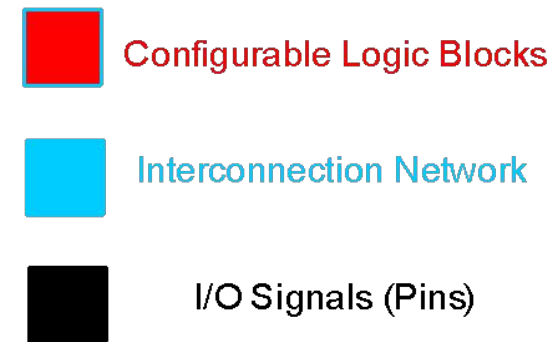 

COMPUTATIONAL STRUCTURE


SIMPLIFIED CLB STRUCTURE

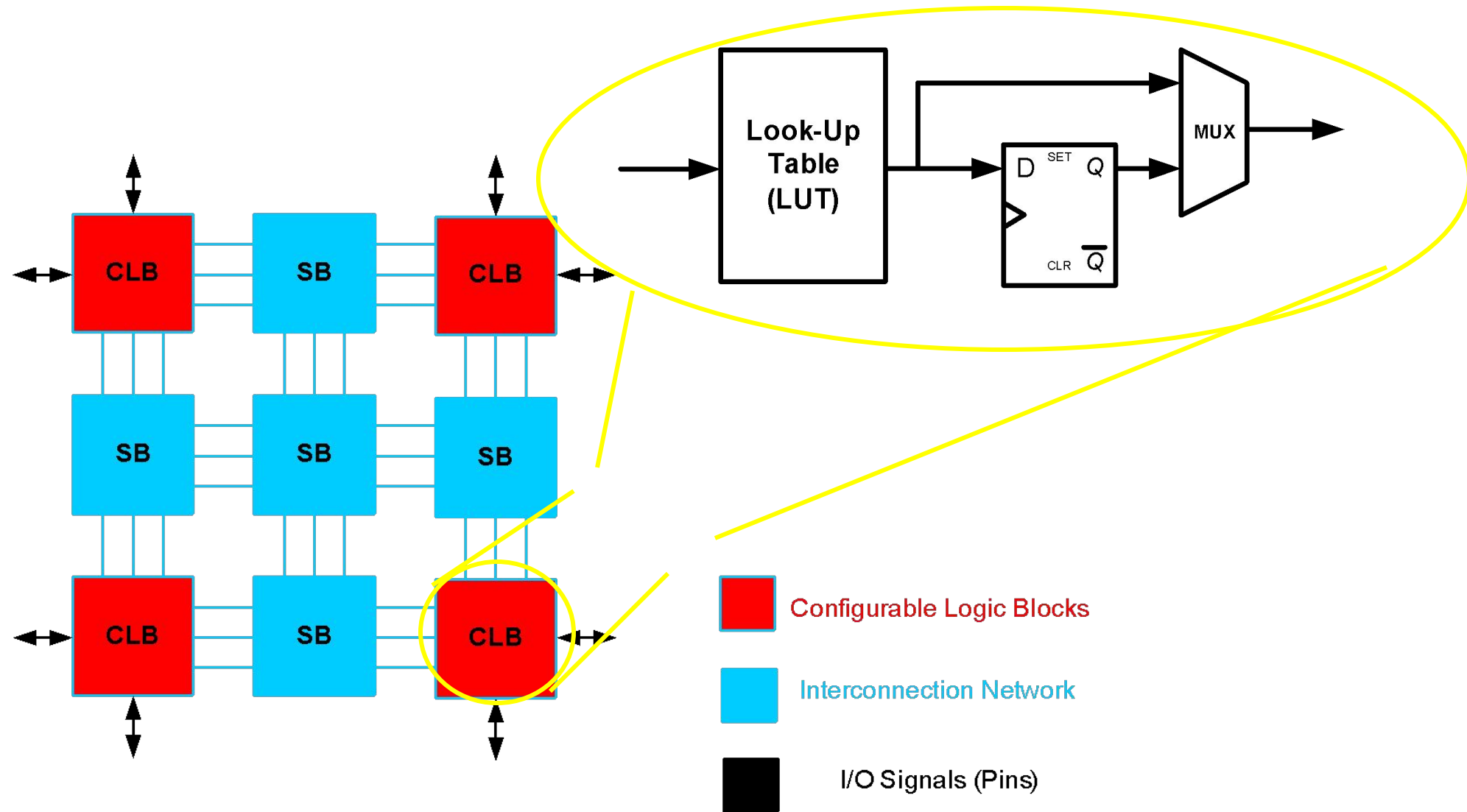

COMPUTATIONAL STRUCTURE



Memory

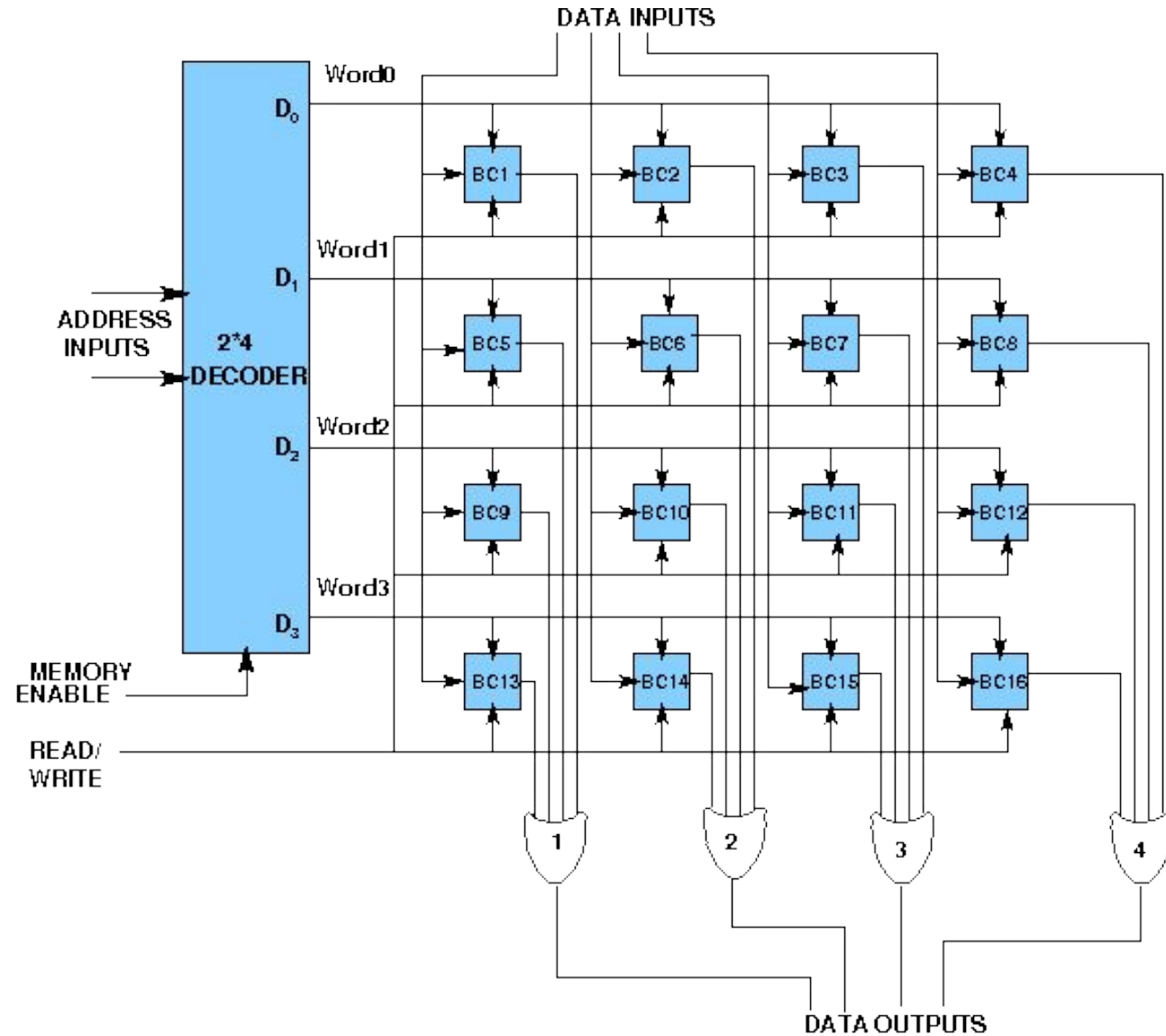- 4 words x 4 bits memory
- Address is n for 2^n words
- Each word is stored in a register (Ex: RAM)




Example: 4-input AND gate

A	B	C	D	O
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

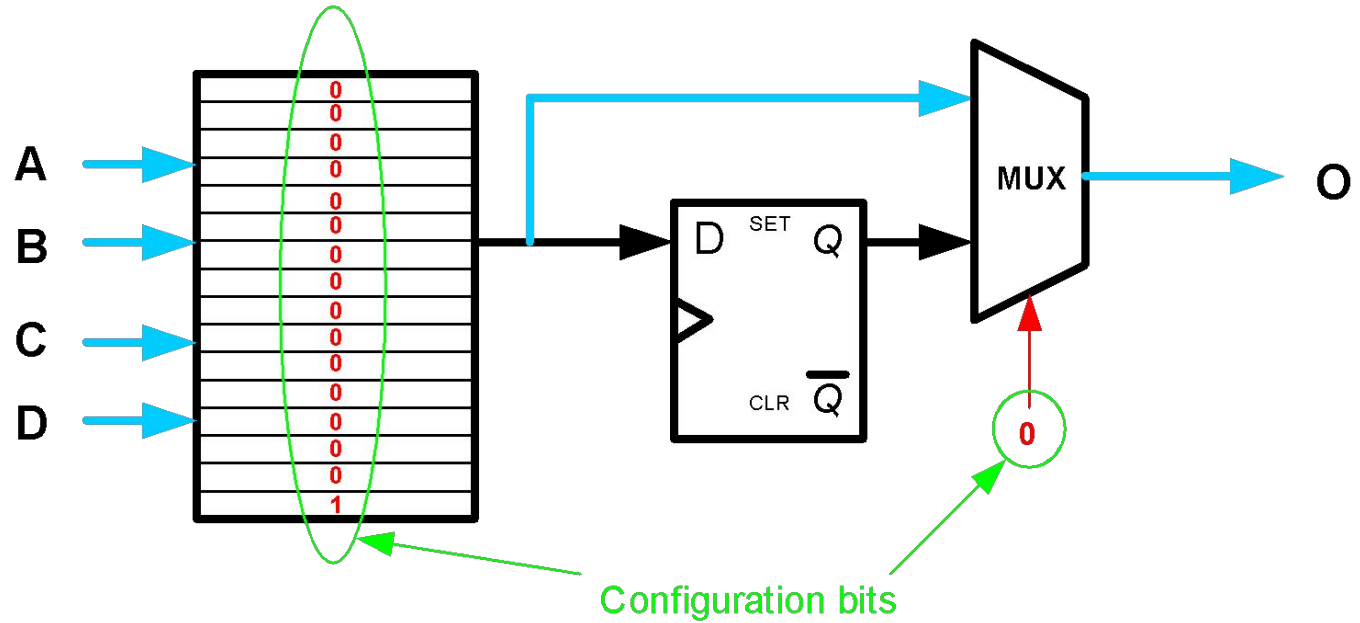 


COMPUTATIONAL STRUCTURE

 Example 2: Find the configuration bits for the following circuit




S	A1	A0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

COMPUTATIONAL STRUCTURE


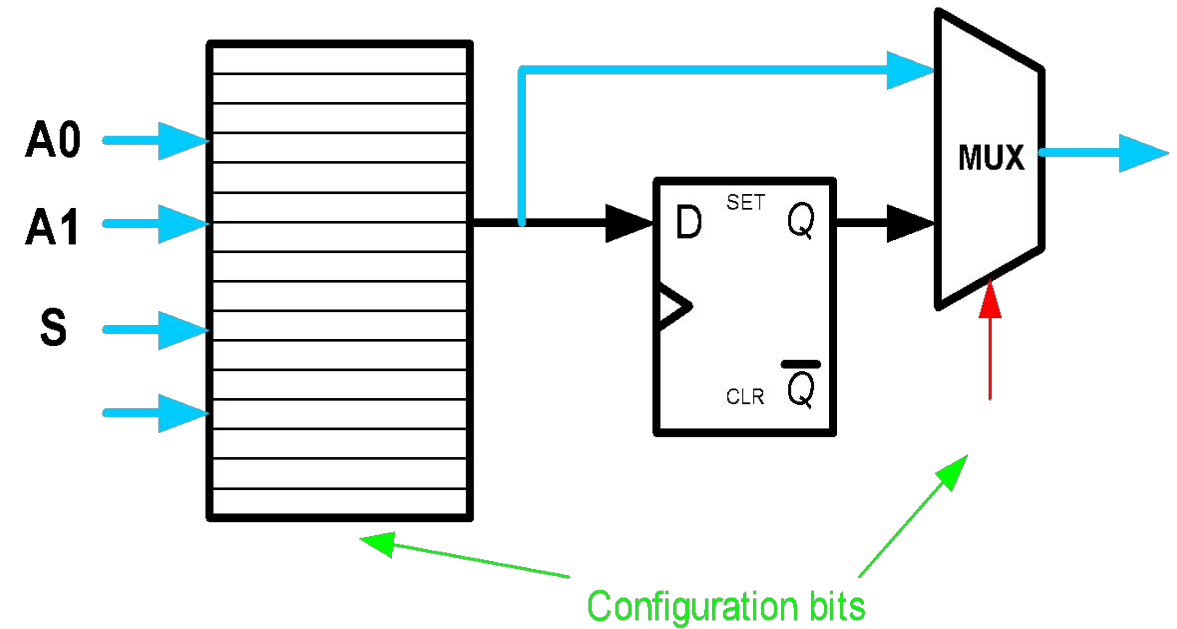


INTERCONNECTION NETWORK


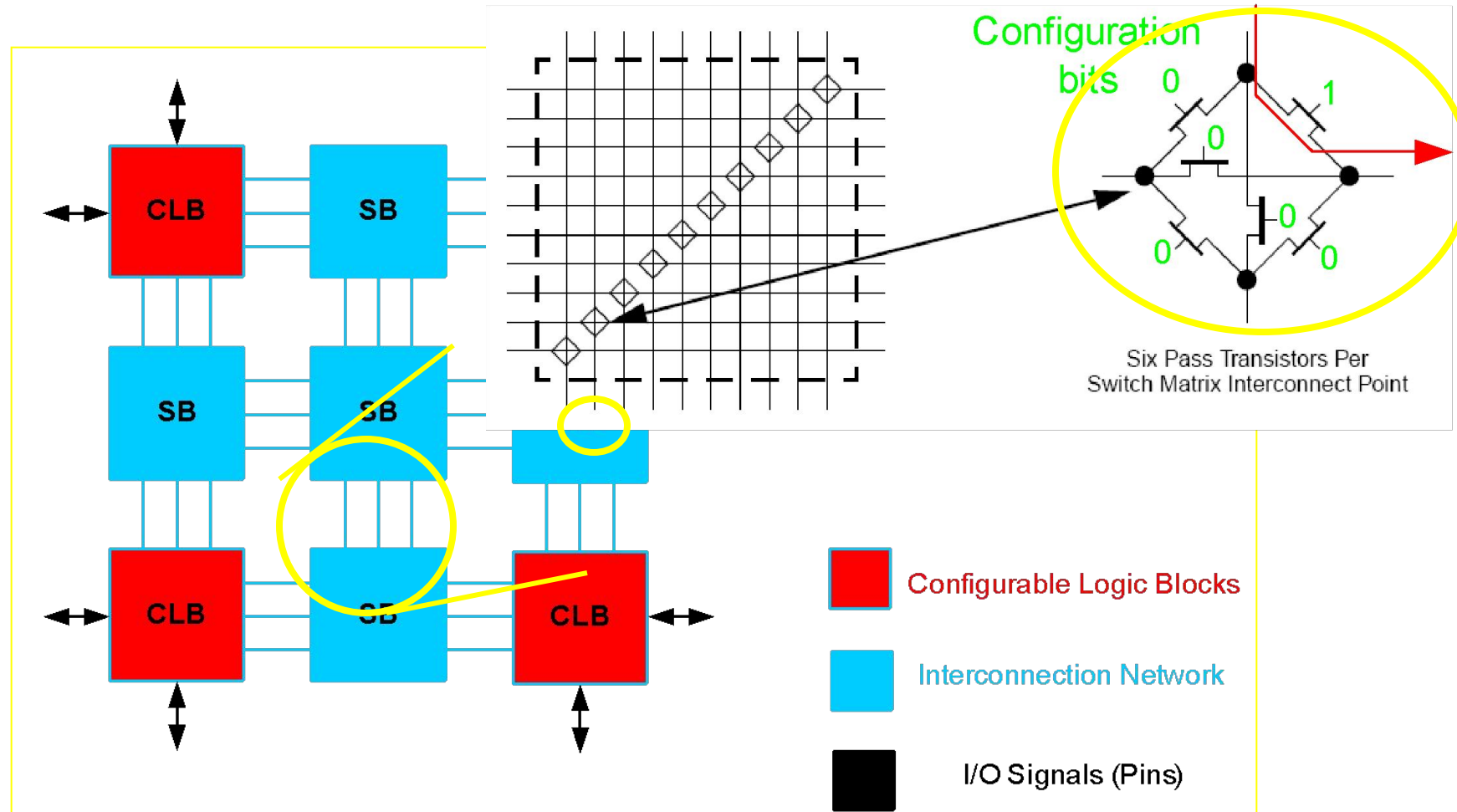


  EXAMPLE 3


- Determine the configuration bits for the following circuit implementation in a 2x2 FPGA, with I/O constraints as shown in the following figure. Assume 2-input LUTs in each CLB.



CLBs Required

  


Placement: Select CLBs

 

COMPUTATIONAL STRUCTURE


Routing: Select path

 

COMPUTATIONAL STRUCTURE


SB1

Configuration bits

 

SB4

Configuration bits

 


A decorative graphic consisting of stylized circuit lines in dark blue and light blue, with small circles at various points, running vertically along the left and right edges of the slide.


Configuration Bitstream:

- The configuration bitstream must include ALL CLBs and SBs, even unused ones
- CLB0: 00011
- CLB1: XXXXX
- CLB2: 01100
- CLB3: XXXXX
- SB0: 000000
- SB1: 000010
- SB2: 000000
- SB3: 000000
- SB4: 000001

Altera DE1 SOC board

 

Cyclone Logic element (LE)

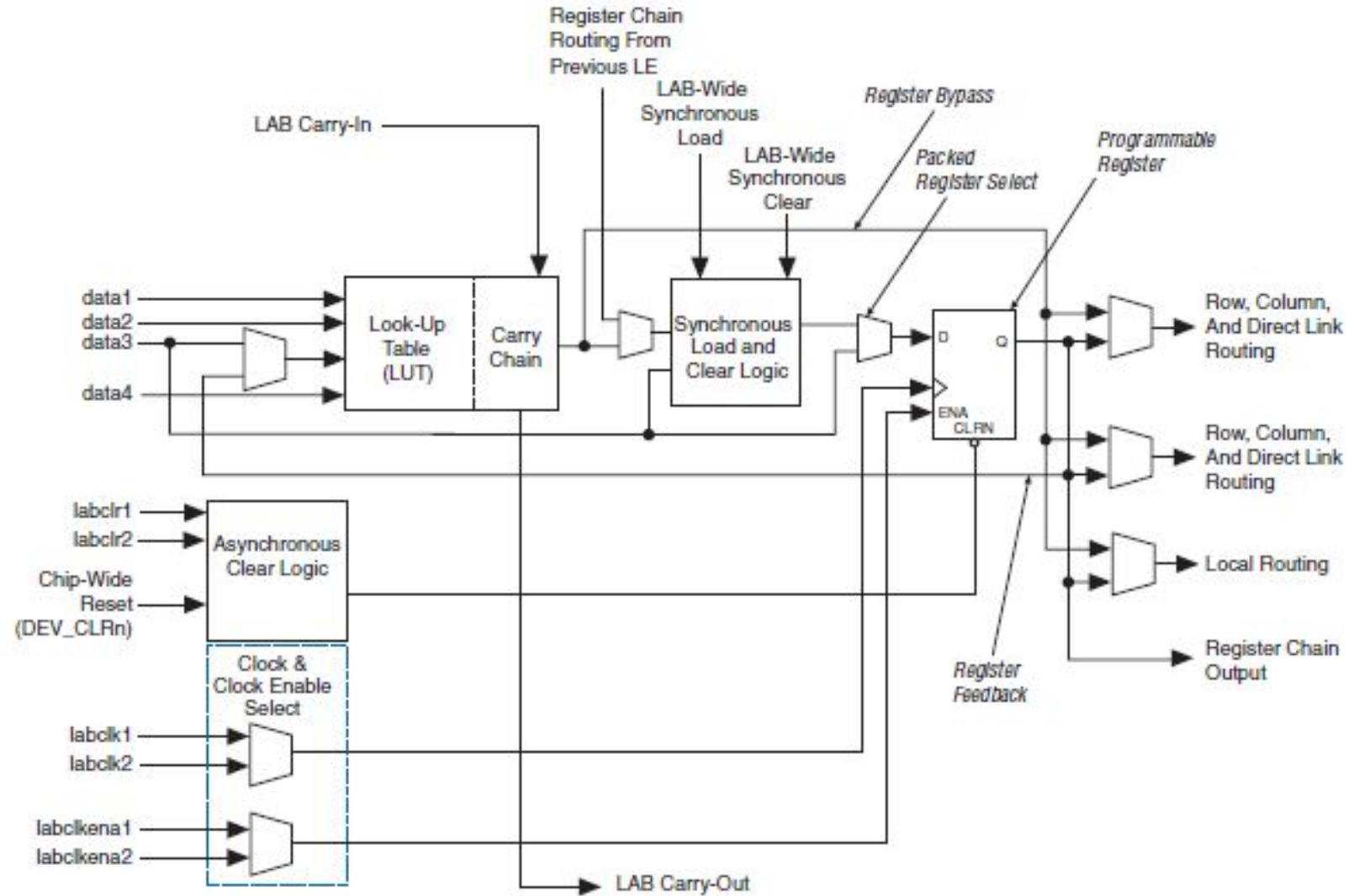

3/23/2020



External links

- <https://www.youtube.com/watch?v=aPXMkJxDS>

Specifications

Features	Cyclone V SE SoC	Cyclone V SX SoC	Cyclone V ST SoC
Processor	Dual-core ARM Cortex-A9 MPCore		
Processor Performance	925 MHz		
Logic Density Range	25 – 110K logic element (LE)		85 – 110K LE
Embedded Memory	5,761 kb		
18 x 19 Multipliers	224		
Maximum Transceivers	N/A	9	
Maximum Transceiver Data Rate (Chip to Chip)	N/A	3.125 Gbps	6.144 Gbps
Memory Devices Supported (Hard Memory Controllers)	x1 32 bit, 400 MHz DDR2/DDR3 with ECC – HPS x1 32 bit, 400 MHz, DDR2/DDR3 - FPGA		
Hard Protocol IP	x2 10/100/1000 EMAC – HPS	x2 10/100/1000 EMAC – HPS x2 PCIe Gen1 - SX x2 PCIe Gen2 - ST	



SUMMARY

- **FPGA** provide the ability to implement logic design with low cost and high speed
- FPGA structure require main blocks are:
 - **Configurable logic blocks**
 - **Interconnect networks**
- Designers may need to alter the **placement and routing** of the selected blocks to improve the design



Thank you Questions?